

Analog

Transistors have 3 mode

- ① Common Emitter

Input → Base

Output → Collector

Ground → Emitter

- ② Common Base

Input → Emitter

Output → Collector

Ground → Base

- ③ Common collector

Input → Base

Output → Emitter

Collector → Ground.

For CB configuration —

- ① DC Source

- ② AC Source

Activity of DC Source

It helps to determine the operation point.

It helps to provide faithful amplification.

Features of Voltage Amplifier —

- ① Input impedance is very high.

- ② Output impedance is low.

- ③ Voltage gain is high.

Features of Current Amplifier —

- ① Input of Current Amplifier.

- ② Output impedance is low.

- ③ Current gain is high.

Power Amplifier

- ① It able to handle large signal voltage.
- ② Rating is very high, rather voltage amplifier.

→ Reason or (3)rd point

→ Doping concentration is very high rather voltage amplifier.

If the signal of 360° passes through a transistor its efficiency will decrease because of no relaxation time for the transistor & the power consumption is very high.

Analog (Banerji Mukherjee)

Types of region in transistor:-

① Active region



- 1.1 Active Forward active region (Bc).
- 1.2 Reverse Active region (BB)

② Cutoff region ($BB \rightarrow$ Rev., $Bc \rightarrow$ Rev.).

③ Saturation region.

($BB \rightarrow$ Forward, $Bc \rightarrow$ Forward).

Circuit Symbol of transistor

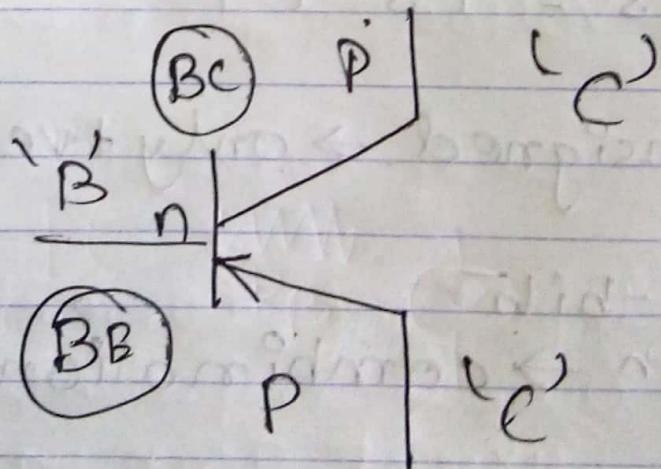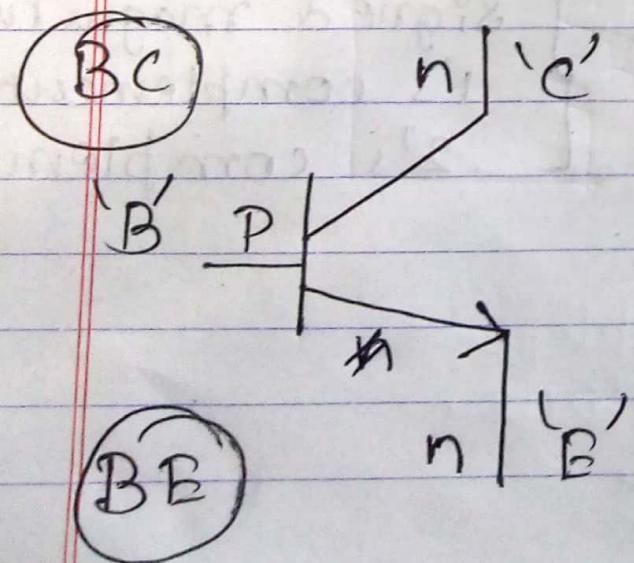

Date: / /

Forward active region
→ act as typical active region.

Note - In active region transistor act as typical amplifier. In cutoff and saturation region act as switch.

Application of transistor :-

- 1) Transistor act as Switch.
- 2) " " " amplifier.
- 3) " " " Oscillator.
- 4) " " " Filter.

For designing amplifiers, needed two types of sources.

e.g. as - DC source, AC source


DC is biasing voltage.

Types of biasing circuit :-

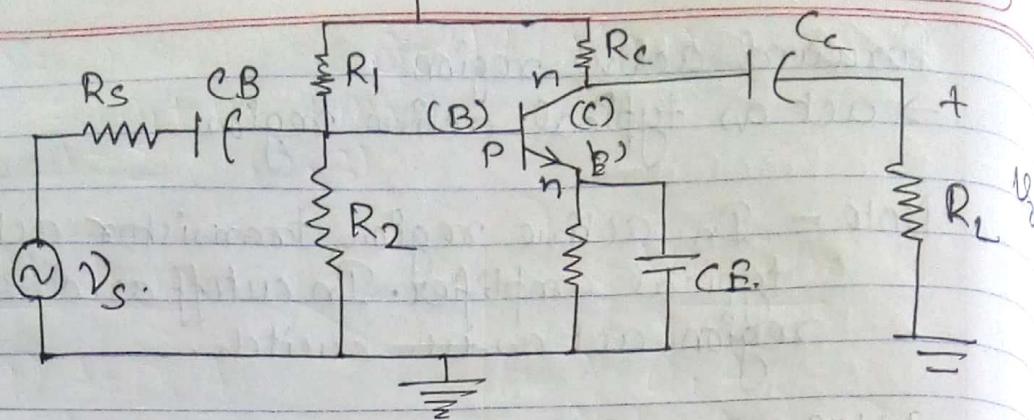- (1) Self biased circuit.
- (2) Collector to base biased circuit.
- (3) Voltage divider biased circuit.

Voltage divider biased is -
obvious because its stability factor (β) is very low.

And its reliability and stability is outstanding.



V_s = source voltage.

R_s = Source resistance.

C_B = Blocking capacitor.

R_1, R_2 = Stabilized resistors.

R_c = Collector " "

R_E = Emitter "


C_E = Bypass capacitor

C_C = Coupling "


R_L = Load resistance.

V_o = Output voltage.

$$\left| \frac{V_o}{V_s} \right| = \text{Gain}$$

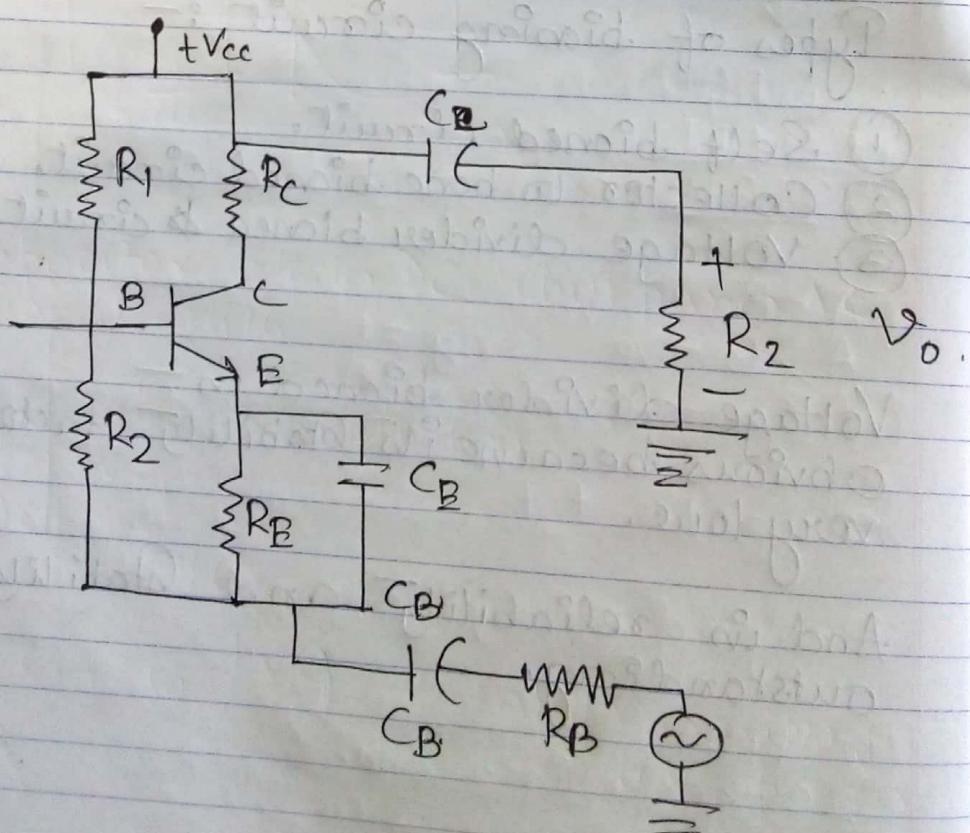

Analog (Bahn & Mülnerjee).

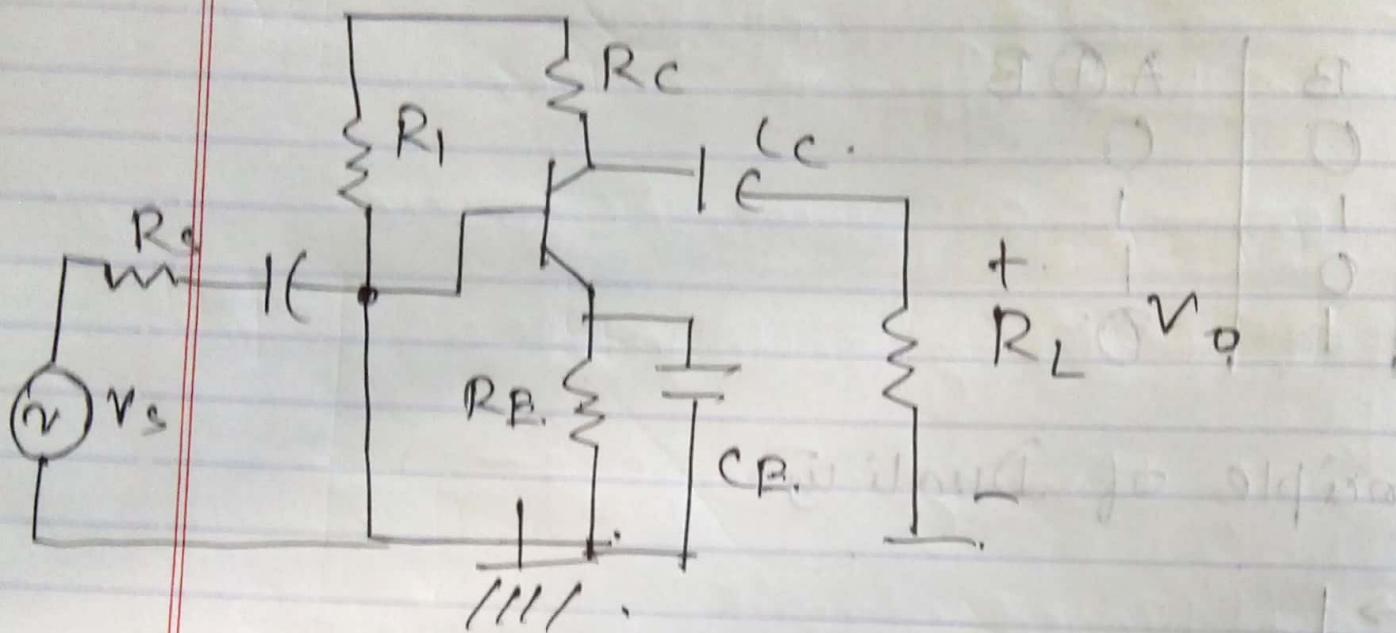


Capacitor blocks DC but passes AC signal easily.

DC load line Analysis

$$|X_C| = \frac{1}{2\pi f C}$$

$$\text{DC, } f=0, |X_C| = \frac{1}{0} = \infty$$

[Capacitor right line open circuit]

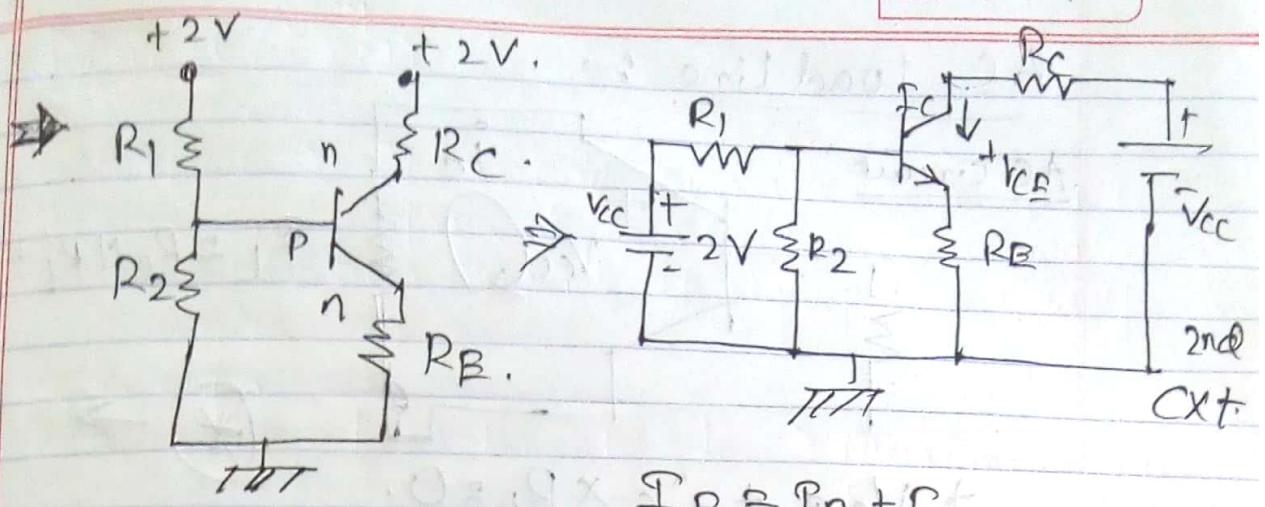

$$I_B = I_B + I_C$$

$$I_B = \frac{I_C}{B} + I_C$$

$$-V_{CC} + I_C \times R_C + V_{CE} + I_E \times R_E = 0$$


$$-V_{CC} + I_C \times R_C + V_{CE} + I_E \times R_E = 0.$$

$$-V_{CC} + I_C (R_C + R_E) + V_{CE} = 0.$$

$$\boxed{I_C (R_C + R_E) + V_{CE} = V_{CC}.}$$





Straight Line

→ DC load Line.

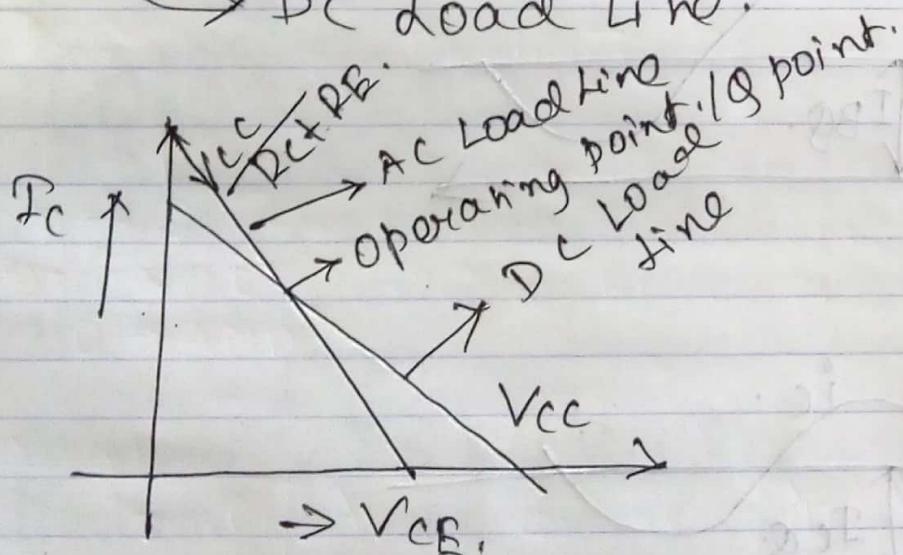


When, $I_C = 0$, $V_{CE} = V_{CC}$.

$$V_{CE} = 0, I_C = \frac{V_{CC}}{R_L + R_C}$$

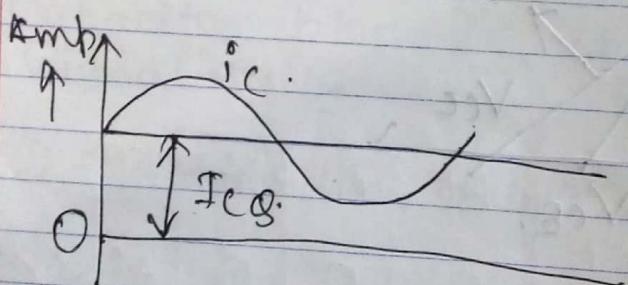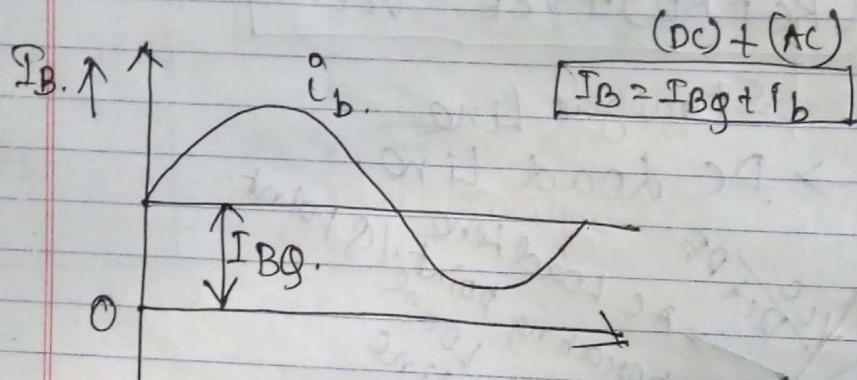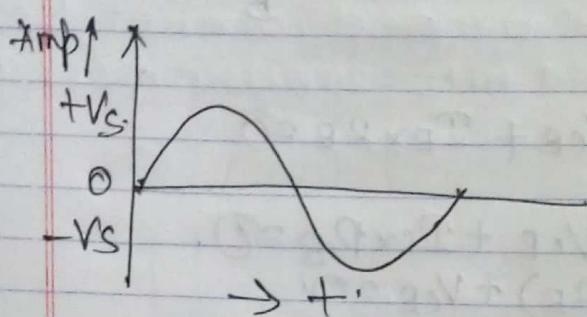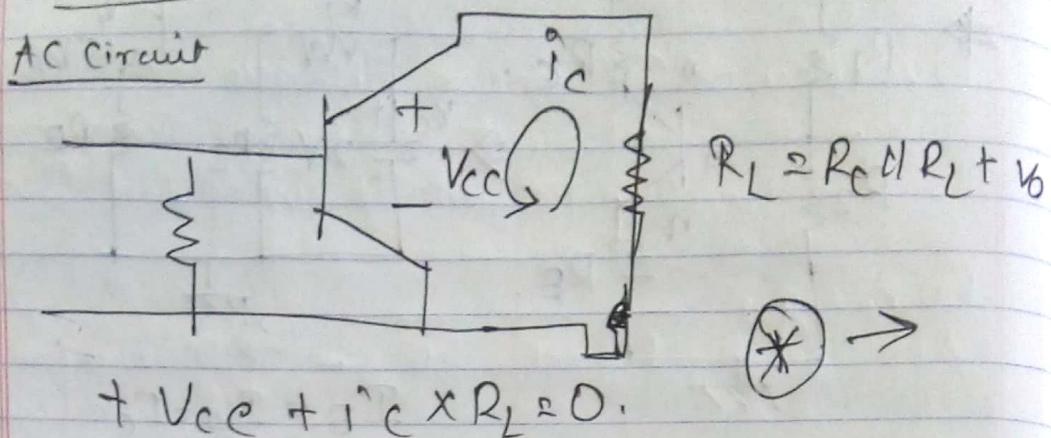AC Load Line

$$\underline{I_C = I_{CQ} + i_c}$$

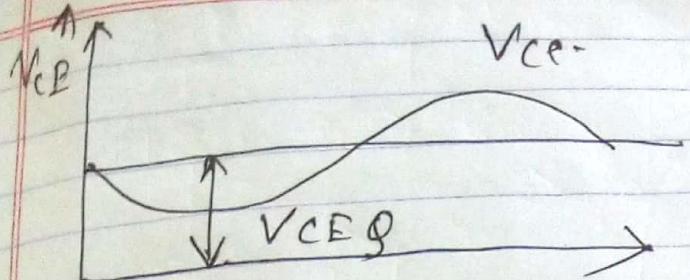

$$V_{CE} = V_{CEg} + V_{ce}$$

$$(V_{CE} - V_{CEg}) + (I_C - I_{Cg}) \times R'_L = 0.$$


$$\frac{V_{CE} + I_C \times R'_L}{V_{CE} + I_{Cg} \times R'_L} = V_{CEg} + V_{CEg} \times R'_L.$$

Case-1, $I_C = 0$, $V_{CE} = V_{CEg} \times R'_L$.

Case-2, $V_{CE} = 0$, $I_C = \frac{V_{CEg}}{R'_L} + V_{CEg}$.

① ~~Case-A~~
~~(θ = 360°)~~

~~AC circuit~~

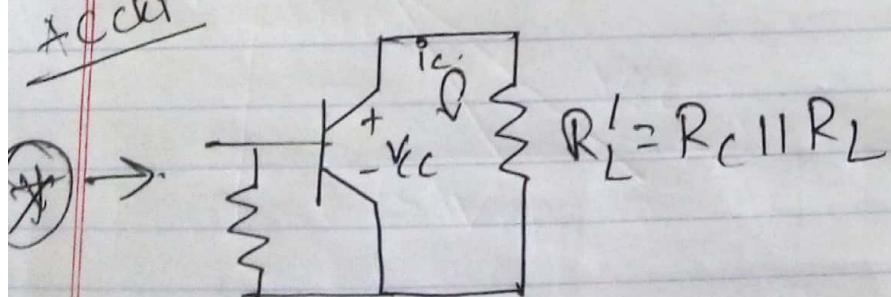

$$+V_{CE} - I_C R'_L = V_{CEg} + V_{CEg} \times R'_L.$$

Case 1, $I_C = 0$, $V_{CE} = V_{CEg} + V_{CEg} \times R'_L$.

$$V_{CE} = 0, I_C = V_{CEg} + V_{CEg} \times R'_L$$

used.

9.6 CLASS A POWER AMPLIFIER

The circuit diagram of a CE-mode class A power amplifier using an *n-p-n* transistor is shown in Fig. 9.8. Of all the three possible transistor configurations, the CE-mode gives the largest power gain. In Fig. 9.8, the amplifier is directly coupled to the load resistance R_L . As the operation is class A, the collector current flows over the entire cycle of the input signal. The blocking capacitor C_1 prevents the interaction between the dc voltage of the base circuit and the ac signal voltage.

The circuit of Fig. 9.8 employs two batteries. A circuit using a single battery and a voltage divider bias is shown in Fig. 8.5. It is assumed here that the battery can deliver the desired power.

Analysis

The analysis uses the output characteristics of the transistor (Fig. 9.9). The transistor must not dissipate a power greater than the allowable limit specified by the manufacturers. For a given ambient temperature, the *maximum power dissipation* is given by

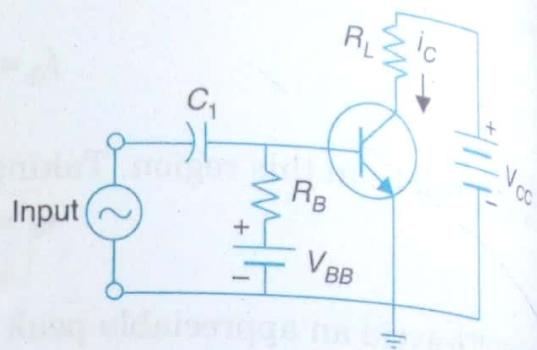


Fig. 9.8 A simple class A power amplifier directly coupled to the load resistance.

$$\begin{aligned}
P_T &= \frac{1}{2\pi} \int_0^{2\pi} v_C(t) i_C(t) d(\omega t) \\
&= \frac{1}{2\pi} \int_0^{2\pi} (V_{CC} - I_{CQ} R_L - I_m R_L \sin \omega t)(I_{CQ} + I_m \sin \omega t) d(\omega t) \\
&= V_{CC} I_{CQ} - I_{CQ}^2 R_L - \frac{1}{2} I_m^2 R_L
\end{aligned} \tag{9.39}$$

In the absence of the signal, $P_T = V_{CC} I_{CQ} - I_{CQ}^2 R_L = V_{CC} I_{CQ}$.

In the presence of the signal, P_T decreases by $\frac{1}{2} I_m^2 R_L = P_{ac}$. Thus, the collector dissipation is a maximum under quiescent conditions.

From Eqs. (9.37) and (9.39), we obtain

$$P_L + P_T = V_{CC} I_{CQ} = P_s, \tag{9.40}$$

where P_s is the dc power supplied by the collector battery. In the presence of the signal, P_L increases by P_{ac} and P_T decreases by P_{ac} , so that the total power ($P_L + P_T$) is a constant equal to the power supplied by the source under quiescent conditions. This is a manifestation of the principle of conservation of energy.

Collector Efficiency

The output power is

$$P_{ac} = \frac{1}{2} I_m V_m = \frac{1}{8} (I_{Cmax} - I_{Cmin})(V_{Cmax} - V_{Cmin}), \tag{9.41}$$

where Eqs. (9.33) and (9.34) have been used. The collector efficiency or the conversion efficiency is

$$\eta = \frac{P_{ac}}{P_s} = \frac{(I_{Cmax} - I_{Cmin})(V_{Cmax} - V_{Cmin})}{8V_{CC} I_{CQ}} \tag{9.42}$$

For ideal collector characteristics,

$V_{Cmin} = 0$, $I_{Cmax} = 2 I_{CQ}$, $V_{Cmax} = V_{CC}$, and $I_{Cmin} = 0$. Hence, Eq. (9.42) gives

$$\eta = \frac{2I_{CQ}V_{CC}}{8I_{CQ}V_{CC}} = 0.25 \tag{9.43}$$

Thus, the maximum efficiency obtainable from a class A power amplifier directly coupled to the load resistance is 25%. The overall efficiency is still smaller since the power taken by the base is not accounted for in the above analysis.

(i) In a double-tuned amplifier, two parallel resonant circuits tuned to the same frequency and having equal effective Q values are used. One tuned circuit is connected to the collector of the first transistor and the other tuned circuit is connected to the base of the second transistor. The two tuned circuits are magnetically coupled and the two transistors are in the CE-mode (Fig. 9.20A).

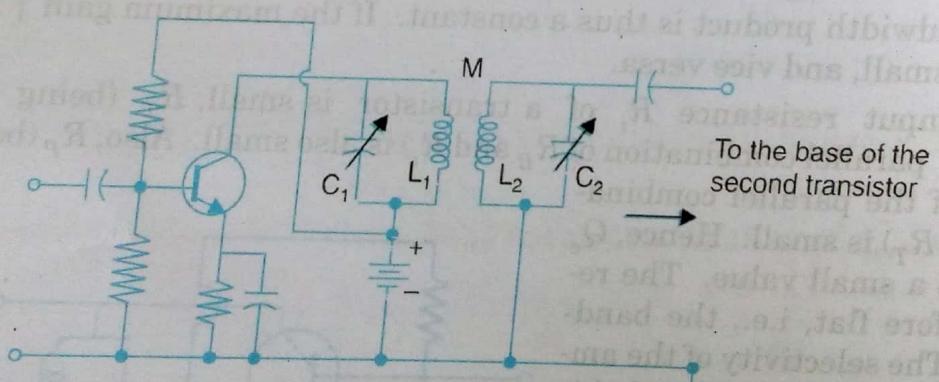


Fig. 9.20A. A double-tuned amplifier.

The output efficiency of an amplifier increases as the operation shifts from class A to class C through class AB and class B. As the output power of a radio transmitter is high and the efficiency is of prime concern, class B and class C amplifiers are used at the output stages in transmitters.

The operations of class B and class C amplifiers are nonlinear since the amplifying elements remain cutoff during a part of the input signal cycle. The nonlinearity generates at the output of the amplifier harmonics of the signal frequency. In the push-pull arrangement where the bandwidth requirement is not limited, these harmonics can be eliminated or reduced. When a narrow bandwidth is desirable, a resonant circuit is employed in class B and class C tuned RF power amplifiers to eliminate the harmonics.

The basic circuit of any class of tuned amplifiers is the same; the value of the base-emitter (BE) junction bias voltage distinguishes between class A, class B or class C operation. For class A operation, the BE junction is forward-biased. In a class B amplifier, the BE junction bias voltage just cancels the barrier potential difference across the junction. In class C operation, the BE junction is reverse-biased.

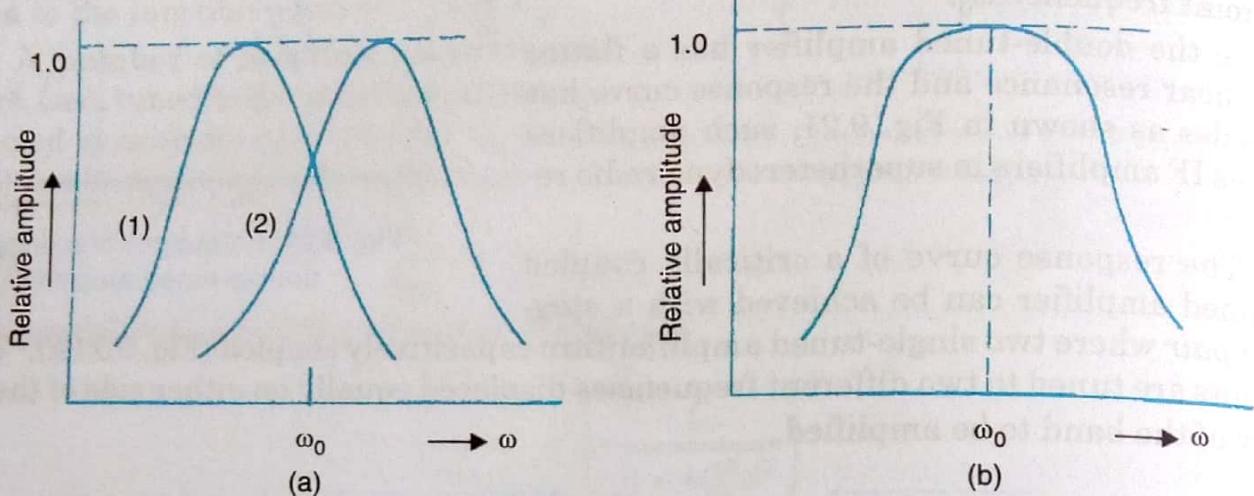


Fig. 9.22 Amplitude response of a stagger-tuned pair: (a) individual responses: curve (1) for the first stage, curve (2) for the second stage : (b) overall response.

Fig. 9.23 depicts the circuit of a class C tuned amplifier in the CE configuration. The source voltage V_{BB} biases the BE junction of the transistor considerably below cutoff. The capacitor C' acts as an RF short. RFC is a radio frequency choke whose high impedance prevents the DC source V_{BB} from shorting the RF input voltage v_i . The signal voltage v_i must have a sufficiently large amplitude so that the BE junction is forward-biased for less than 180° of the input signal cycle. The transistor starts conducting when v_i exceeds V_L where V_L is V_{BB} plus the transistor cutin voltage. The conduction stops when v_i drops below V_L . The collector current therefore consists of a series of pulses, there being one pulse for each cycle of the input signal. The peaks of these pulses resemble the peaks of the input sine wave and the duration of each pulse is less than half the period of the input signal. Clearly, harmonics of the input signal are present in the collector current. As the parallel resonant circuit, providing the load impedance, is tuned to the input frequency and has a high Q , the load impedances at the harmonic frequencies are negligibly small compared to that at the resonant frequency. Thus only the fundamental component of the load voltage corresponding to the input frequency is significant at the output. The output voltage across the tuned circuit is sinusoidal and has the same frequency as that of the input signal.

The instantaneous value of the collector voltage is a minimum when the collector current is a maximum. So, the ac component of the collector voltage is sinusoidal and 180° out of phase with the input signal voltage. The waveforms for a sinusoidal input signal voltage in a class C amplifier is shown in Fig. 9.24.

A class C tuned amplifier operates at the resonant frequency f_0 of the tank circuit, where $f_0 = \frac{1}{2\pi\sqrt{LC}}$. The bandwidth is given by $B = \frac{f_0}{Q_e}$, where Q_e is the effective Q of the tank circuit.

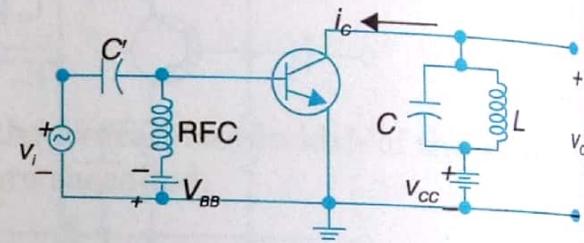


Fig. 9.23 A class C tuned amplifier

If I_1 is the peak value of the fundamental component of the collector current, the ac output power for maximum drive is $P_{ac} = V_{cc} I_1/2$. The dc power supplied by the collector supply is $P_s = I_o V_{cc}$ where I_o is the average value of the collector current. The efficiency is $\eta = P_{ac}/P_s = I_1/(2I_o)$. Since I_o is quite small, η is very high (about 90%).

A class C tuned amplifier can be used as a *frequency multiplier* if the resonant circuit is tuned to a harmonic of the input signal.


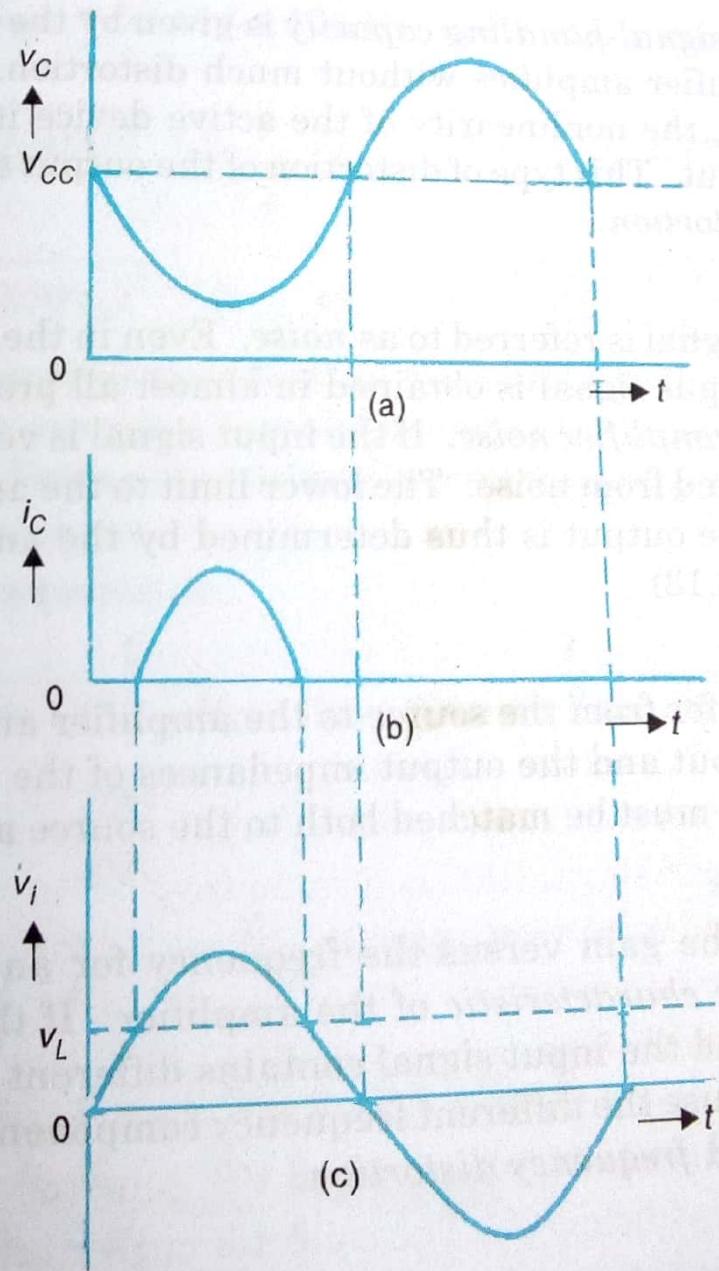
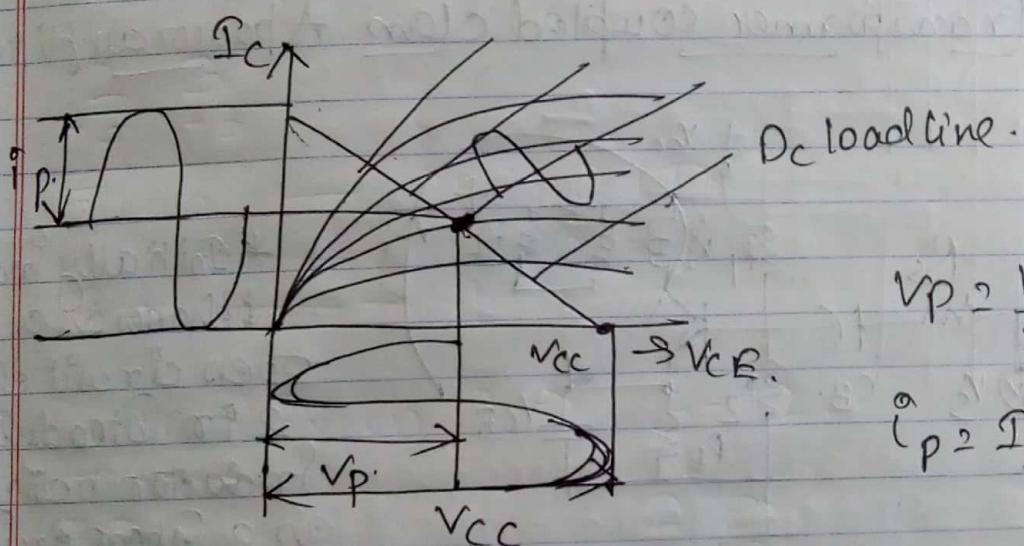


Fig. 9.24 Typical waveforms in class C tuned amplifiers:
 (a) collector voltage v_c against time t , (b) collector current i_c against t , and
 (c) input ac voltage v_i as a function of t .

PB(Analog)
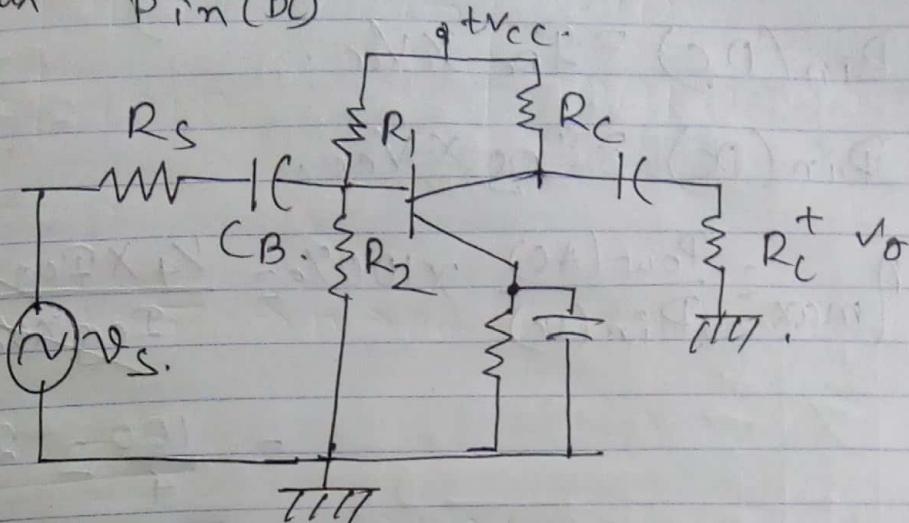
$$\eta_{\max} = \frac{P_{out}(AC)}{P_{in}(DC)} \times 100\%.$$



$$V_p = \frac{V_{cc}}{2}$$

$$i_p = P_{CG}$$

$$P_{out}(AC) = i_c(rms) \times V_{CE}(rms)$$

$$I_C = P_{CG} + i_p \cos \omega t$$

$$V_{CE} = V_{CEG} + V_p \cos(\omega t + \pi)$$

Agaⁿ,

$$P_{out}(AC) = i_c(rms) \times V_{CE}(rms)$$

$$= i_p \sqrt{2} \times V_p \sqrt{2} \times \frac{1}{2} \times P_{CG} \times \frac{V_{cc}}{2}$$


$$P_{out(AC)} = \frac{1}{4} \times I_{CQ} \times V_{CC}$$

$$P_{in(DC)} = I_{DC} \times V_{CC}$$

$$P_{in(DC)} = I_{CQ} \times V_{CC}$$

$$\eta_{max} = \frac{P_{out(AC)}}{P_{in(DC)}} \times 100\% = \frac{\frac{1}{4} \times I_{CQ} \times V_{CC}}{I_{CQ} \times V_{CC}} \times 100\% = \frac{100}{4} = 25\%$$

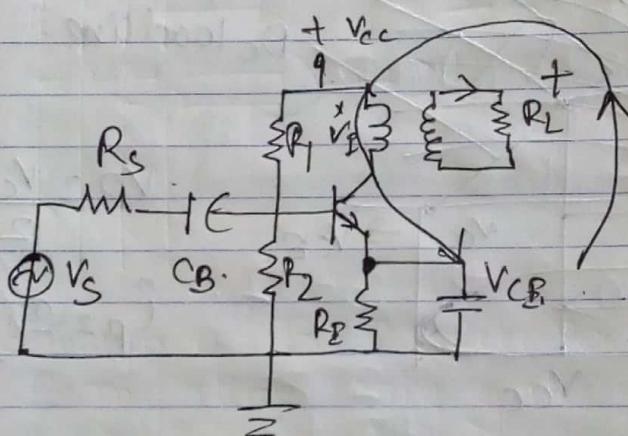Transformer coupled class A power amplifier




* Initially it behaves as an open circuit element & in steady state it induces current in the primary coil which acts as a short circuit element.

$$-V_{CC} + V_T + V_{CB} = 0$$

$$V_{CB} \approx V_{CC} - V_T$$

V_{CB} is constant.

DC load line.

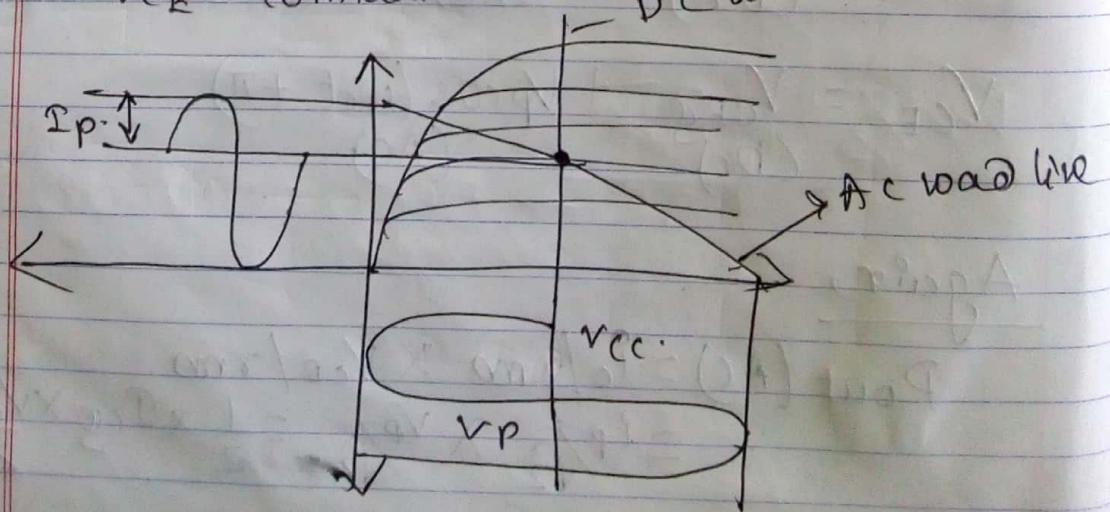

@Orunayan@

pioneerpaper.com
Page: / /
Date: / /

$$\boxed{V_p = V_{cc}} \\ \boxed{i_p = I_{cg}}$$

$$P_{out}(AC) = i_c^2 / r_m \times V_{ce} / r_m \\ = i_p^2 / \sqrt{2} \times \frac{V_p}{\sqrt{2}} \\ = \frac{1}{2} \times i_p \times V_p.$$

$$P_{out}(AC) = \frac{1}{2} \times i_{cg} \times V_{cc}.$$

$$P_{in}(DC) = P_{dc} \times V_{cc}.$$

$$\boxed{P_{in}(DC) = P_{cg} \times V_{cc}}.$$

$$\eta_{max} = \frac{P_{out}(AC)}{P_{in}(DC)} \times 100.$$

$$= \frac{\frac{1}{2} \times i_{cg} \times V_{cc} \times 100}{P_{cg} \times V_{cc}}.$$

$$= \frac{100}{2} = 50\%.$$

1 [2ND MID SEM]


Feedback & Oscillator

The term 'Feedback' implies transfer of energy from the output of a system to the input. It is the position of the input signal of a amplifier is fed back and super imposed on the input signal, the performance of the amp changes significantly. The amplifier is then said to be a feedback amplifier.

Types of feedback:-

- i) +ve feedback \rightarrow It's unstable & gain is infinite.
- ii) -ve \rightarrow It's stable & gain is low


Block Diagram of Feedback Amplifier:

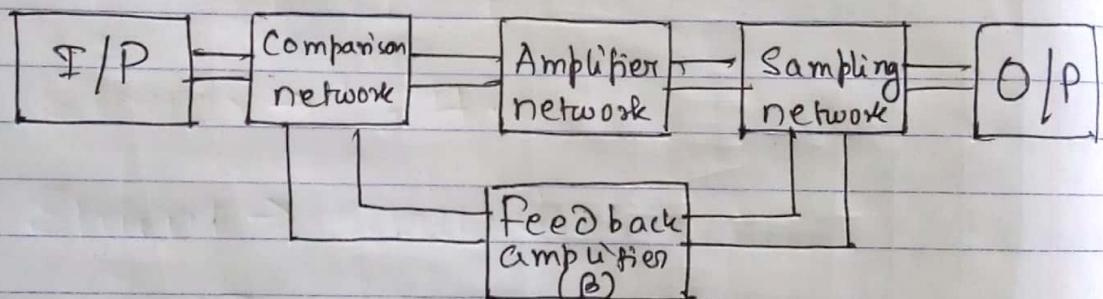

Feedback Topologies:-

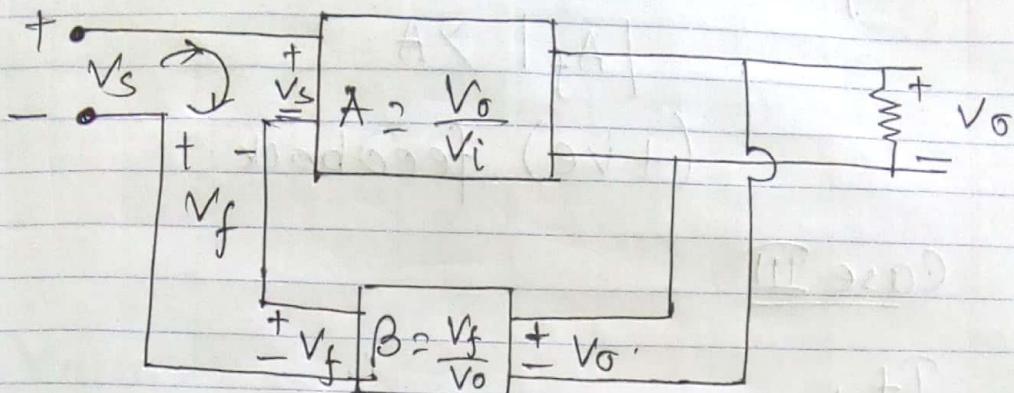- 1) Voltage Series Feedback.
- 2) Voltage Shunt "
- 3) Current Series "
- 4) Current Shunt "

* General expression for obtaining gain of feedback amplifier.



$$\text{Overall Transfer Gain } (A_f) = \frac{V_o}{V_s} .$$

$$A = \frac{V_o}{V_i}$$

$$\Rightarrow A/V_o = A \cdot V_i$$

$$\Rightarrow V_o = A(V_s - V_f)$$

$$[V_o = V_s - V_f]$$

$$\Rightarrow V_o = AV_s - AV_f$$

$$\beta = \frac{V_f}{V_o}$$

$$\Rightarrow V_o = A \cdot V_s - A \cdot V_f$$

$$\Rightarrow V_o + A\beta V_o = A \cdot V_s$$

$$\Rightarrow [V_o(1 + A\beta) = A \cdot V_s]$$

$$\boxed{\frac{V_o}{V_s} = \frac{A}{1 + A\beta} = A_f}$$

Case - 1

$$\text{If } |1 + A\beta| > 1$$

$|A_f| < A$, then -ve feedback

Case - II

If $|1 + A\beta| < 1$.

$|A_f| > A$.


(+ve) feedback.

Case III

If, $|1 + A\beta| = 0$

$\downarrow |A_f| = \infty$

Then it treated as a oscillator

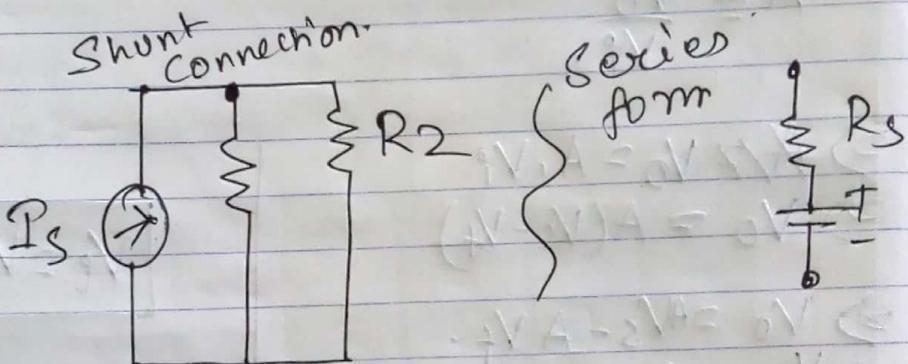


Series \rightarrow $V_o H$.

Shunt \rightarrow Current.


$V_o H \rightarrow$ Parallel

Current \rightarrow Series.


VOLTAGE SHREWS

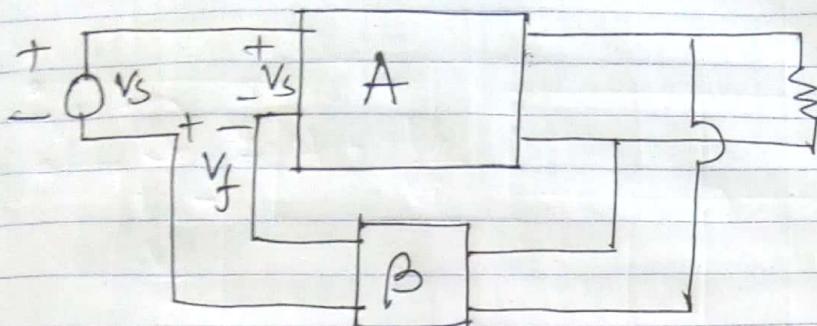

Voltage Shunt:

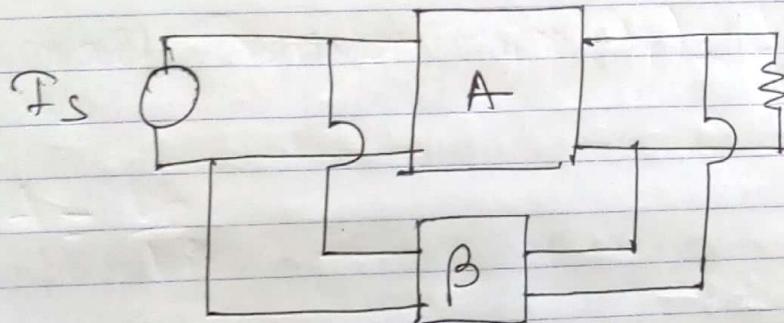


Current Series:-

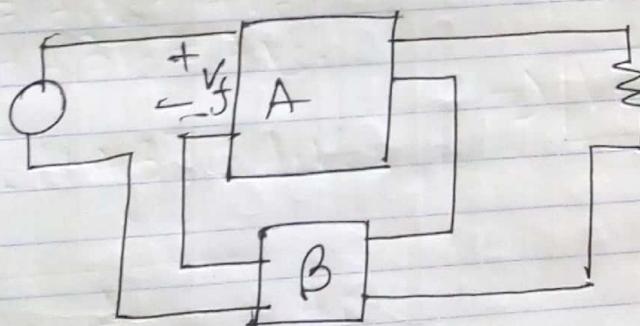

Topologies of feedback

- 1) Voltage Series feedback
- 2) Voltage Shunt feedback
- 3) Current Series feedback
- 4) Current Shunt feedback

Voltage Series feedback

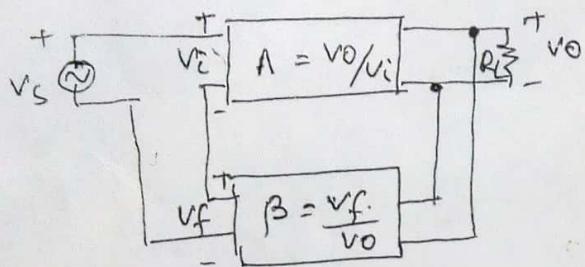

$$V_f = \beta V_o \quad \text{as} \quad \beta = \frac{V_f}{V_o}$$

$$V_i = V_s - V_f = V_s - \beta V_o$$

$$A = \frac{V_o}{V_i}$$

$$V_o = A V_i = A (V_s - \beta V_o)$$

$$A_f = \frac{V_o}{V_s}$$

$$\textcircled{2} \quad V_o = A (V_s - \beta V_o)$$


$$= A V_s - A \beta V_o$$

$$\text{or } V_o + A \beta V_o = A V_s \Rightarrow V_o (1 + A \beta) = A V_s$$

$$\therefore A_f = \frac{V_o}{V_s} = \frac{A}{1 + A \beta}$$

∴ the feedback reduces the gain by a factor $(1 + A \beta)$ [negative feedback].

Voltage Shunt

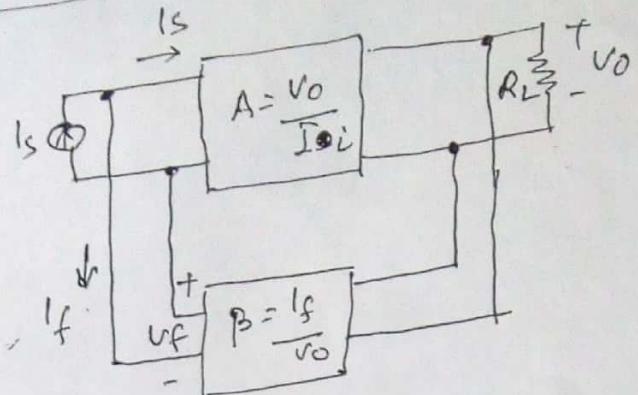

I_i → input current
 I_f → feedback current
 I_s → source current
 V_o → op. v. voltage

$$A = \frac{V_o}{I_i} \quad \text{or} \quad V_o = A I_i$$


$$\beta = \frac{I_f}{V_o} \quad \text{or} \quad I_f = \beta V_o$$

$$\therefore I_s = I_i + I_f = I_i + \beta V_o$$

$$\begin{aligned} A_f &= \frac{V_o}{I_s} = \frac{V_o}{I_i + \beta V_o} \\ &= \frac{A I_i}{I_i + \beta V_o} = \frac{A}{1 + A\beta} \end{aligned}$$

amplifier gain is reduced by a factor $(1 + A\beta)$ due to feedback.

Current Series feedback

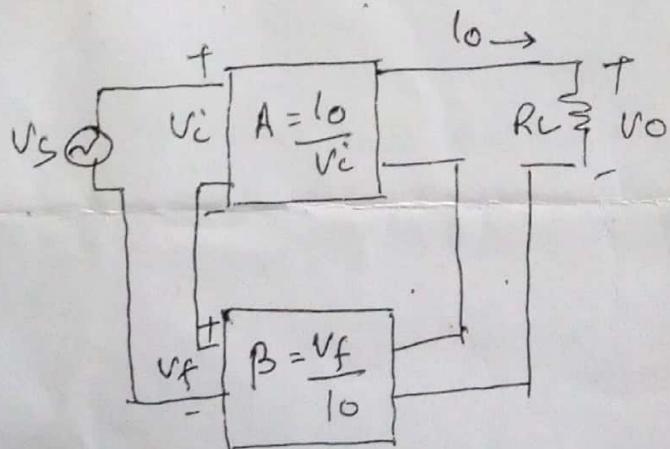


$$A_f = \frac{I_o}{I_s} = \frac{I_o}{I_c + I_f} = \frac{I_o}{I_c + \beta I_o}$$

$$= \frac{A(c)}{I_c + \beta A(c)} = \frac{A}{1 + \beta A}$$

The gain is reduced by a factor $(1 + \beta)$ when feedback is introduced.

Oscillator

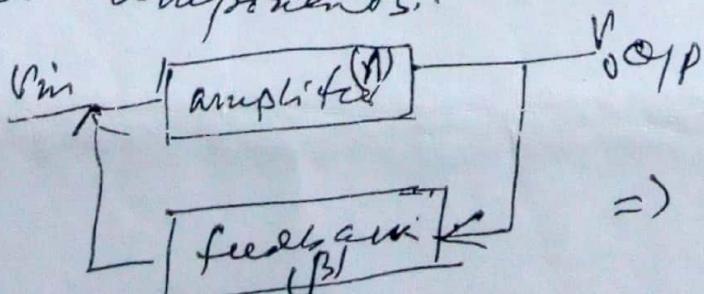An oscillator is a circuit which produces continuous, repeated, alternating waveform without any input. This circuit converts unidirectional current flow from a DC source into an alternating waveform which is of the desired frequency, as decided by circuit components.



=> Typical oscillator.


Oscillator :-

A system that consist of active and passive circuit element to produce a sinusoidal or other repetitive wave form.

Types of oscillator :-

- i) AF (0-20 kHz)
- ii) RF (20 kHz - 30 kHz)
- (a) Wien Wien Bridge
- (b) phase-shift.
- (a) Hartley
- (b) Colpitts
- (c) Tuned.

Block diagram of oscillator :-

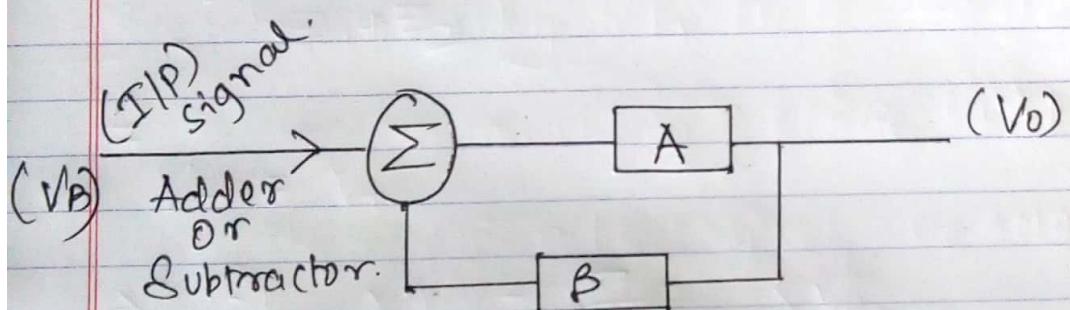

$$\frac{V_o}{V_s} = \frac{A}{1 - A\beta}$$

Condition of oscillator :-


$$1 - A\beta = 0 \Rightarrow A\beta = 1$$

loop gain:

(0° or ± 360°).

PB (Analog)

(Wein Bridge Oscillator).

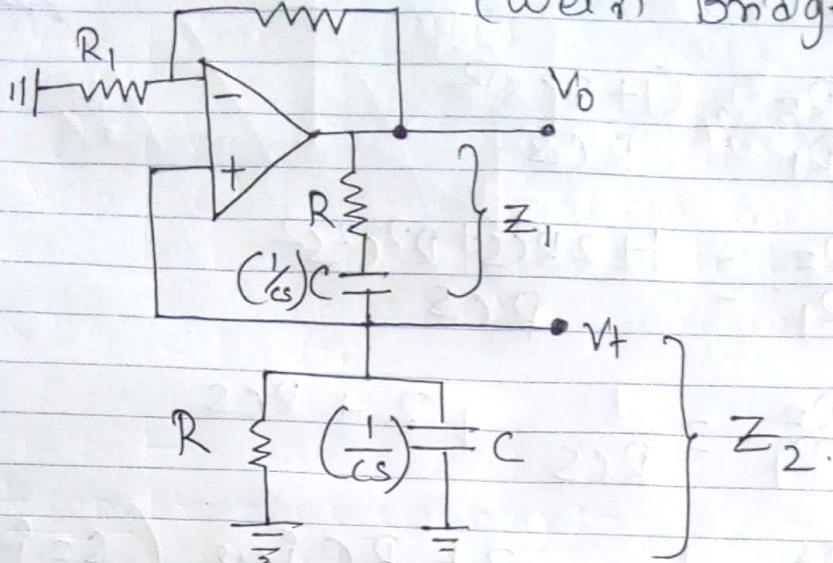

$$V_- = \frac{R_1}{R_1 + R_F} \times V_0$$

$$V_+ = \left(\frac{Z_2}{Z_1 + Z_2} \right) \times V_0.$$

$$V_- = V_+$$

$$\Rightarrow \frac{R_1}{R_1 + R_F} \times V_0 = \frac{Z_2}{Z_1 + Z_2} \times V_0$$

$$\Rightarrow \frac{R_1 + R_F}{R_1} = \frac{Z_1 + Z_2}{Z_2}$$

$$\Rightarrow \frac{R_F}{R_1} + 1 = \frac{Z_1}{Z_2} + 1$$

$$\Rightarrow Z_1 = R + 1/c_s.$$

$$\Rightarrow Z_2 = \frac{R \times 1/c_s}{R + 1/c_s} = \frac{R}{c_s} \times \frac{c_s}{R c_s + 1} = \frac{R}{R c_s + 1}.$$

$$\frac{R_F}{R_1} \geq \frac{Z_1}{Z_2} \Rightarrow \frac{R_F}{R_1} = \frac{(1+RCS)}{CS} \times \frac{(1+RCS)}{RCS}$$

$$\Rightarrow \frac{R_F}{R_1} \geq \frac{(1+RCS)^2}{RCS}$$

$$\Rightarrow \frac{R_F}{R_1} = \frac{1 + 2RCS + R^2C^2S^2}{RCS}$$

$$\Rightarrow \frac{R_F}{R_1} \geq \frac{1}{RCS} + 2 + RCS$$

$$\Rightarrow \frac{R_F}{R_1} = \frac{1}{RCSj\omega} + 2 + RCj\omega \quad (S=j\omega)$$

$$\Rightarrow \frac{R_F}{R_1} + 0 \cdot j = 2 + j \left(RC\omega - \frac{1}{RC\omega} \right)$$

$$\frac{R_F}{R_1} \geq 2$$

$$RC\omega = \frac{1}{RC\omega} \geq 0$$

$$\Rightarrow RC\omega \geq \frac{1}{RC\omega} \Rightarrow R^2C^2\omega^2 \geq 1$$

$$\Rightarrow \omega = \frac{1}{RC} \Rightarrow 2\pi f = \frac{1}{RC}$$

$$\Rightarrow \boxed{f = \frac{1}{2\pi RC}}$$

11.7 PHASE-SHIFT OSCILLATOR

Fig. 11.6 shows the circuit of a phase-shift oscillator. The dc operating point of the transistor in the active region of its characteristics is established by the resistors R_1 , R_2 , R_L and R_E , and the supply voltage $-V_{cc}$. The capacitor C_E is a bypass capacitor.

As the transistor is in the CE configuration, it introduces a phase difference of 180° between its input and output voltages. The three sections of RC network give an extra phase difference of 180° so that the net phase shift around the loop is 0° or 360° .

For convenience, the three RC sections are taken to be identical. The resistance in the last

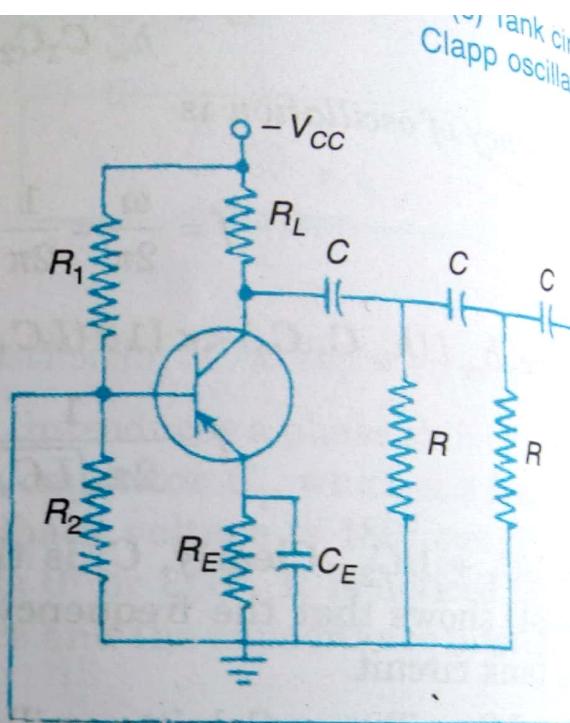


Fig. 11.6 Circuit of a phase-shift

section is $R' = R - h_{ie}$. The input resistance h_{ie} of the transistor is added to R' , thus giving a net resistance R . The RC phase-shift networks constitute the frequency determining circuit.

Analysis

The resistances R_1 and R_2 are large and therefore have no effect on the AC operation of the circuit. The $R_E - C_E$ parallel combination is also absent from the AC equivalent circuit of Fig. 11.7(a) due to the negligible impedance offered by this combination to ac. As $1/h_{oe} \gg R_L$, one can neglect $1/h_{oe}$ which is in parallel with R_L . Also, h_{re} being small, $h_{re} V_2$ can be omitted. The equivalent circuit of Fig. 11.7(a) then simplified to the circuit of Fig. 11.7(b) where the current source is replaced by its equivalent voltage source.

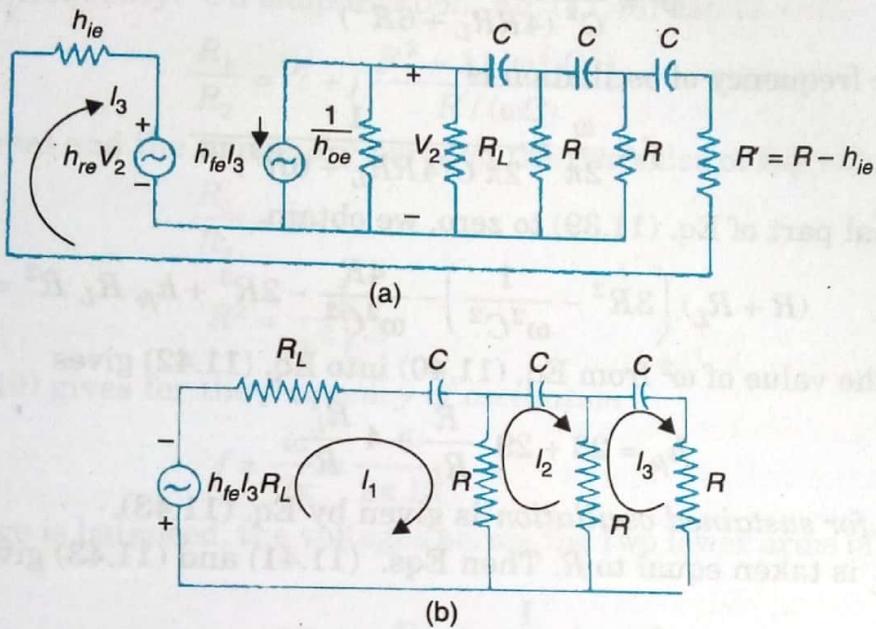


Fig. 11.7 (a) AC equivalent circuit of Fig. 11.6, (b) Simplified AC equivalent circuit with $h_{re} V_2$ and $1/h_{oe}$ neglected.

Kirchhoff's voltage law equations for the three loops in Fig. 11.7(b) are respectively written as

$$\left(R_L + R - \frac{j}{\omega C} \right) I_1 - RI_2 + h_{fe} R_L I_3 = 0 \quad (11.35)$$

$$-RI_1 + \left(2R - \frac{j}{\omega C} \right) I_2 - RI_3 = 0 \quad (11.36)$$

$$0I_1 - RI_2 + \left(2R - \frac{j}{\omega C} \right) I_3 = 0 \quad (11.37)$$

and where ω is the angular frequency of oscillation. Since the currents I_1 , I_2 , and I_3 are nonzero, the determinant of the coefficients of I_1 , I_2 , and I_3 in Eqs. (11.35) through (11.37) must vanish. Thus

$$\begin{vmatrix} R_L + R - \frac{j}{\omega C} & -R & h_{fe} R_L \\ -R & 2R - \frac{j}{\omega C} & -R \\ 0 & -R & 2R - \frac{j}{\omega C} \end{vmatrix} = 0. \quad (11.38)$$

or,

$$\left(R_L + R - \frac{j}{\omega C} \right) \left(3R^2 - j \frac{4R}{\omega C} - \frac{1}{\omega^2 C^2} \right) - R^2 \left(2R - \frac{j}{\omega C} \right) + h_{fe} R_L R^2 = 0 \quad (11.39)$$

Equating the imaginary part of Eq. (11.39) to zero, we get

$$-4R \frac{(R + R_L)}{\omega C} - \frac{1}{\omega C} \left(3R^2 - \frac{1}{\omega^2 C^2} \right) + \frac{R^2}{\omega C} = 0$$

or,

$$\omega^2 = \frac{1}{C^2 (4RR_L + 6R^2)} \quad (11.40)$$

Therefore, the frequency of oscillation is

$$f = \frac{\omega}{2\pi} = \frac{1}{2\pi C (4RR_L + 6R^2)^{1/2}} \quad (11.41)$$

Putting the real part of Eq. (11.39) to zero, we obtain

$$(R + R_L) \left(3R^2 - \frac{1}{\omega^2 C^2} \right) - \frac{4R}{\omega^2 C^2} - 2R^3 + h_{fe} R_L R^2 = 0 \quad (11.42)$$

Substituting the value of ω^2 from Eq. (11.40) into Eq. (11.42) gives

$$h_{fe} = 23 + 29 \frac{R}{R_L} + 4 \frac{R_L}{R} \quad (11.43)$$

The condition for sustained oscillation is given by Eq. (11.43).

Ordinarily, R_L is taken equal to R . Then Eqs. (11.41) and (11.43) give

$$f = \frac{1}{2\sqrt{10} \pi CR}, \quad (11.44)$$

and

$$h_{fe} = 56. \quad (11.45)$$

Hence, for sustained oscillations, the transistor should have an h_{fe} of 56 when $R_L = R$.

Phase-shift oscillators are commonly employed in the AF range. The frequency of oscillation here can be changed by using a ganged variable capacitor with three sections. To vary the frequency, the capacitances of the three sections are varied simultaneously. As conventional variable capacitors have capacitances in the range 50 pF to 500 pF, the frequency of oscillation can be altered in the ratio 10 : 1. For a greater variation of frequency, different resistors of resistances differing by a factor of 10 are employed.

11.4 TUNED-COLLECTOR OSCILLATOR

Fig. 11.2 (a) depicts the circuit diagram of a tuned-collector oscillator. The dc operating point of the transistor in the active region of its characteristics is determined by the resistances R_1 , R_2 and R_E and the collector supply voltage $-V_{CC}$. The emitter by-pass capacitor C_E shunts the alternating components so that R_E does not appear in the ac equivalent circuit of Fig. 11.2(b).

As the transistor is in the CE configuration, it gives a phase shift of 180° between its input and output voltages. The transformer introduces another 180° phase shift needed for oscillation.

The frequency-determining circuit is made up by the capacitor C together with the transformer primary inductance L . The LC tuned circuit connected to the collector accounts for the name 'tuned-collector oscillator'. The LC tuned circuit is called the *tank circuit* because this circuit determines or *stores* the frequency of oscillation. Furthermore, it is a reservoir of current, and stores electric and magnetic energies.

The resistance R_B is effectively in parallel with the resistance R_2 . Since R_B is very large, its effect on the dc operating point is small. The main purposes served by R_B are to (i) reduce the loading of the collector circuit by the low input resistance of the transistor, (ii) introduce regenerative feedback just required to sustain oscillations, and (iii) decrease the input nonlinear distortion.

Analysis

The resistance R_B is chosen to be much larger than h_{ie} of the transistor and ωL_s , where ω is the angular frequency of oscillation and L_s is the transformer secondary inductance. As a result, the current I_1 in the transformer secondary is so small that it induces a negligible voltage in the transformer primary. In other words, the large value of R_B ensures that the LC tuned circuit is not significantly loaded. Therefore, the frequency of oscillation $f [= \omega/(2\pi)]$ is approximately given by the natural resonant frequency of the LC tank circuit. Thus,

$$f \approx \frac{1}{2\pi\sqrt{LC}} \quad (11.2)$$

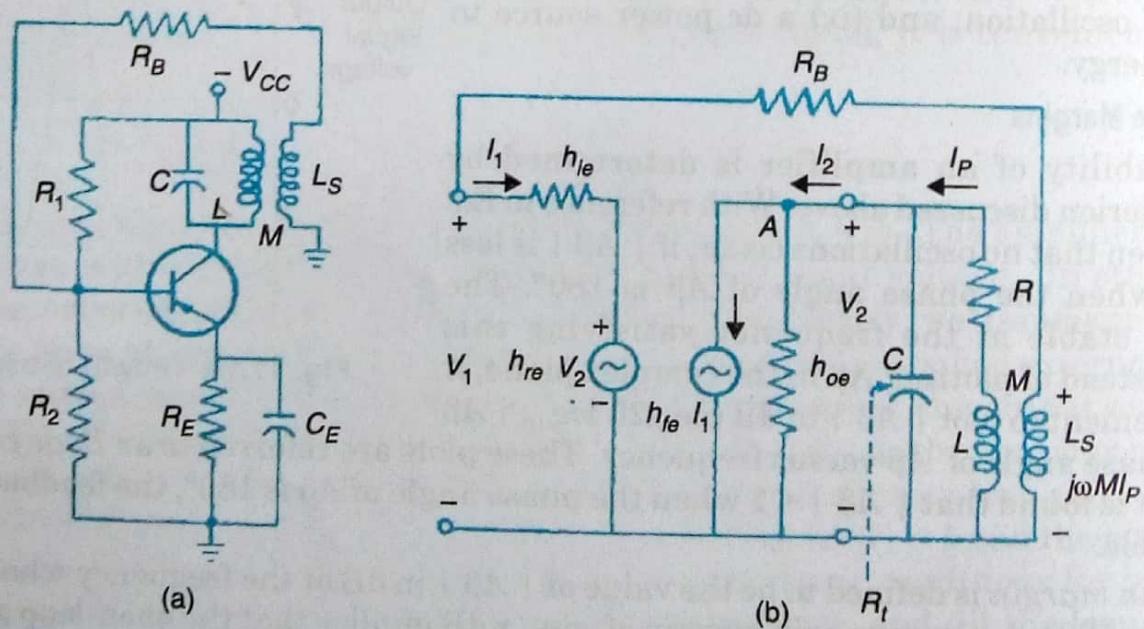


Fig. 11.2 (a) Circuit diagram of a tuned-collector oscillator (b) Its ac equivalent circuit.

The frequency of oscillation can be changed by varying either L or C , or both. Usually, the capacitor C is changed for practical convenience. With available values of L and C , tuned-collector oscillators generate oscillations in the RF range.

supply voltage $-V_{cc}$. The capacitor C_B is the blocking capacitor, while C_E is the bypass capacitor. Since the transistor is in the CE configuration, a phase shift of 180° exists between the input and output voltages. The output voltage appears across the tank circuit connected to the collector. The feedback voltage is a part of the output voltage, namely, V_1 appearing across the inductance L_1 . The phase shift between the feedback voltage and the output voltage is 180° . Therefore, the total phase shift around the loop is 0° or 360° . The frequency-determining circuit is constituted by the capacitor C , and the inductors L_1 and L_2 .

Analysis

The ac operation of the circuit is not affected by the resistances R_1 and R_2 which are large. The resistance R_E is also ineffective in the ac behaviour due to the bypass capacitor C_E . The hybrid model ac equivalent circuit of the Hartley oscillator is depicted in Fig. 11.4(a).

We apply Thevenin's theorem looking towards the left at the terminals X, Y in the circuit of Fig. 11.4(a). The current source $h_{fe} I_1$ in shunt with the resistance $(1/h_{oe})$ is replaced by an equivalent Thevenin voltage source of generated voltage $(h_{fe} I_1/h_{oe})$ and internal resistance $(1/h_{oe})$. The equivalent circuit with this Thevenin representation is given in Fig 11.4(b). We neglect here, for simplicity, the mutual inductance between L_1 and L_2 .

From Fig. 11.4(b), we obtain for the voltage across the terminals X, Y

$$V_2 = \frac{1}{h_{oe}} I_2 - \frac{h_{fe}}{h_{oe}} I_1 \quad (11.13)$$

The Kirchhoff voltage law equations for the loops (1), (2), and (3) in Fig. 11.4(b) are, respectively,

$$\left(h_{ie} + j\omega L_1 - \frac{h_{fe} h_{re}}{h_{oe}} \right) I_1 + \frac{h_{re}}{h_{oe}} I_2 - j\omega L_1 I_3 = 0, \quad (11.14)$$

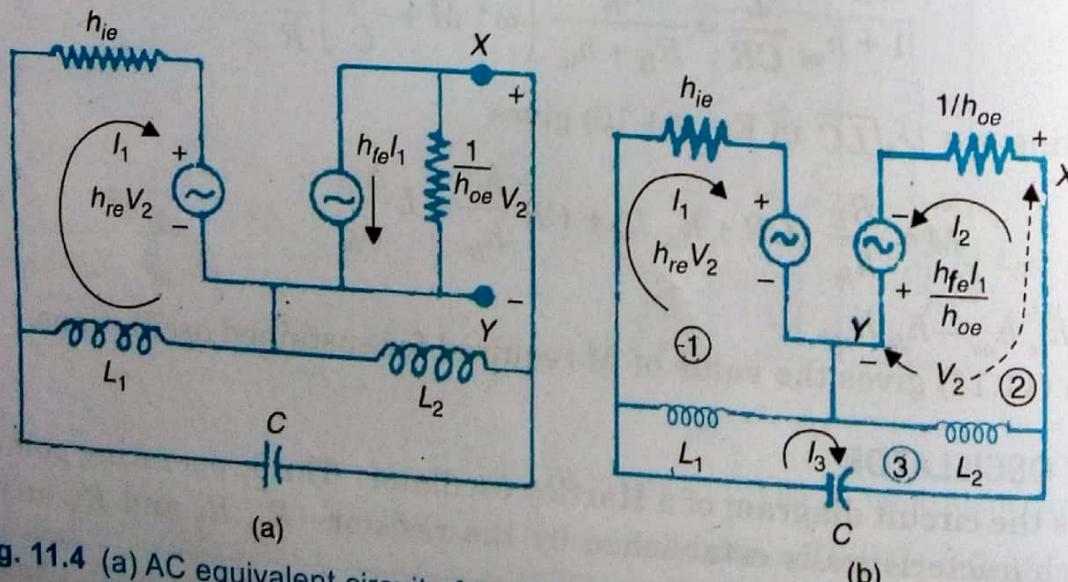


Fig. 11.4 (a) AC equivalent circuit of the Hartley oscillator, (b) AC equivalent circuit with the current source replaced by an equivalent voltage source.

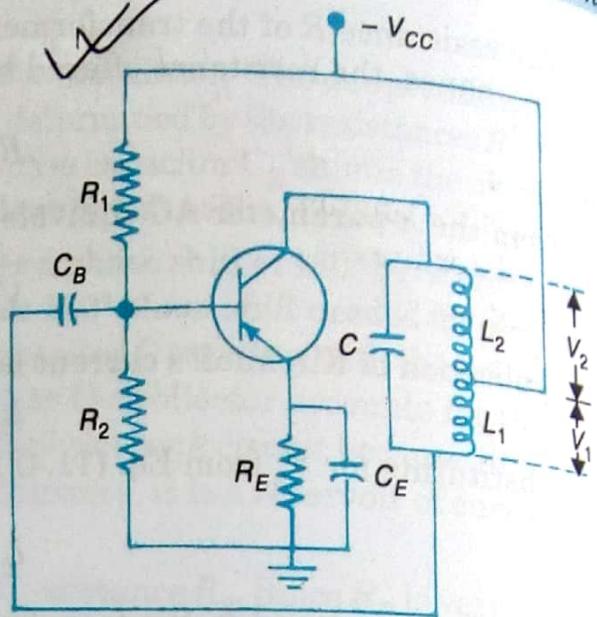


Fig. 11.3 A Hartley oscillator circuit.

In practice, $h_{oe} L_1 L_2 / h_{ie} \ll C(L_1 + L_2)$, so that Eq. (11.25) gives

$$f \approx \frac{1}{2\pi \sqrt{C(L_1 + L_2)}} = \frac{1}{2\pi \sqrt{LC}}, \quad (11.26)$$

where $L (= L_1 + L_2)$ is the total inductance of the tank-circuit coil. Thus the circuit gives oscillations at nearly the resonant frequency of the tank circuit.

As mentioned earlier, we have neglected in the above analysis the mutual inductance M between L_1 and L_2 . It can be shown that, when M is incorporated, L_1 and L_2 in Eqs. (11.23) and (11.26) are respectively replaced by $(L_1 + M)$ and $(L_2 + M)$.

Hartley oscillators usually generate oscillations in the RF range since the required values of L and C are convenient from practical considerations. The frequency of oscillation can be altered by varying L or C or both. The capacitance C can be easily changed, but smooth variations of L over a large range are inconvenient. So, for a smooth variation of frequency, capacitive tuning is preferred. Since variable capacitors have capacitances in the range 50 pF to 500 pF, Eq. (11.26) shows that the frequency of oscillation can be changed in the ratio 3 : 1.

11.6 COLPITTS OSCILLATOR

A Colpitts oscillator circuit is shown in Fig. 11.5(a). The dc operating point of the transistor in the active region of its characteristics is established by the resistors R_1 , R_2 , R_L , and R_E , and the supply voltage $-V_{CC}$. The capacitor C_B blocks the dc current flow from the collector to the base of the transistor through the coil of inductance L . The capacitor C_E is a bypass capacitor. The reactances of C_E and C_B are negligible at the frequency of oscillation. The inductance L and the capacitances C_1 and C_2 constitute the frequency-determining network.

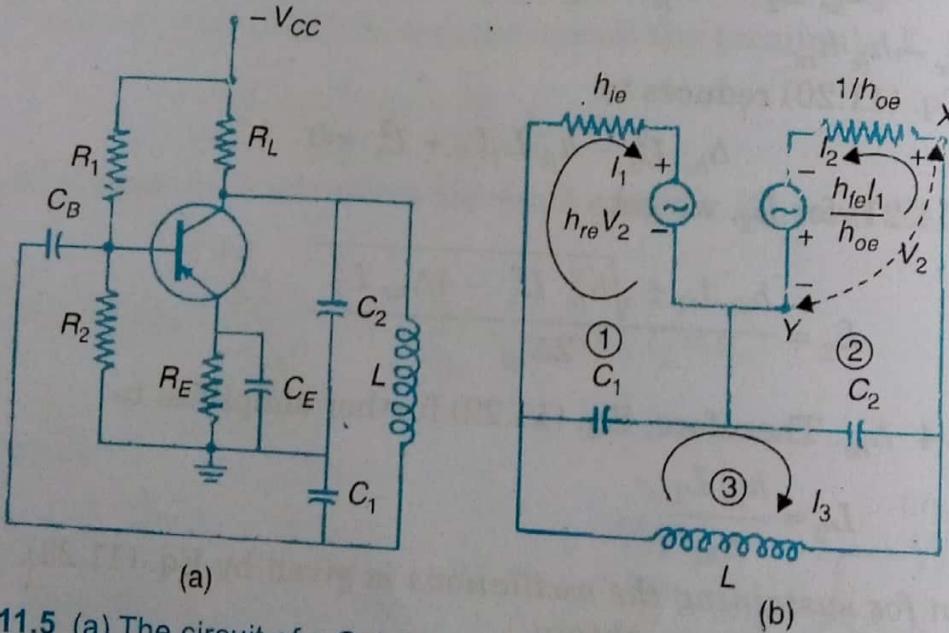


Fig. 11.5 (a) The circuit of a Colpitts oscillator, (b) Its AC equivalent circuit.

The transistor being in the CE configuration, introduces a phase shift of 180° between its input and output voltages. The voltage across the capacitor C_1 , which is a fraction of the output voltage, is the feedback voltage. As the feedback voltage is 180° out of phase with the output voltage, the phase shift around the loop is 0° or 360° . It is noticed that Hartley and Colpitts oscillators are similar with the inductance and the capacitance interchanged.

Analysis

Since R_1 and R_2 are large resistances, they do not affect the ac operation of the circuit. Also, R_E , being shunted by C_E which bypasses the ac, is excluded from the AC equivalent circuit, shown


11.10 MULTIVIBRATORS

The multivibrator is a relaxation oscillator generating nonsinusoidal waveforms. Basically, the multivibrator is a two-stage amplifier or oscillator operating in two *modes* or *states*. Each amplifier stage feeds back the other such that the active element of one stage is driven to saturation and the other to cut off. A new set of actions, producing the opposite effects, then follows. Thus the saturated stage becomes cutoff and the cutoff stage saturates. The operation of the multivibrator is based on the fact that *no two active elements have exactly identical characteristics.*

There are three classes of multivibrators: *astable*, *bistable*, and *monostable*. The *astable* or the *free-running* multivibrator alternates automatically and continuously between two states at a rate dictated by the circuit components. The *bistable* multivibrator, also referred to as an *Eccles-Jordan*, or a *flip-flop* multivibrator, operates in two states but requires an external trigger pulse to change from one state of operation to the other. The circuit continues in the existing state till a trigger pulse is applied. The *monostable* multivibrator, also known as a *single-shot*, a *single-swing* or a *one-shot* multivibrator, has a *normal* or a *quiescent state* and a *transient state*. When an external trigger pulse is applied, the circuit goes over to the transient state from the quiescent state, and automatically returns to its initial quiescent state after a time interval determined by the circuit components.

(1) Astable Multivibrator

An astable multivibrator using two similar transistors Q_1 and Q_2 is shown in Fig. 11.11. The circuit is basically two symmetrical CE amplifier stages, each supplying a feedback signal to the other. The transistor Q_1 is forward-biased by the supply voltage V_{CC} and the resistance R_3 while Q_2 is forward-biased by V_{CC} and the resistance R_2 . The collector-emitter voltages of Q_1 and Q_2 are determined respectively by the load resistances R_1 and R_4 together with V_{CC} . The capacitor C_1 couples the output of Q_1 to the input of Q_2 , whereas C_2 couples the output of Q_2 to the input of Q_1 . In practice, $R_1 = R_4$, $R_2 = R_3$, and $C_1 = C_2$.

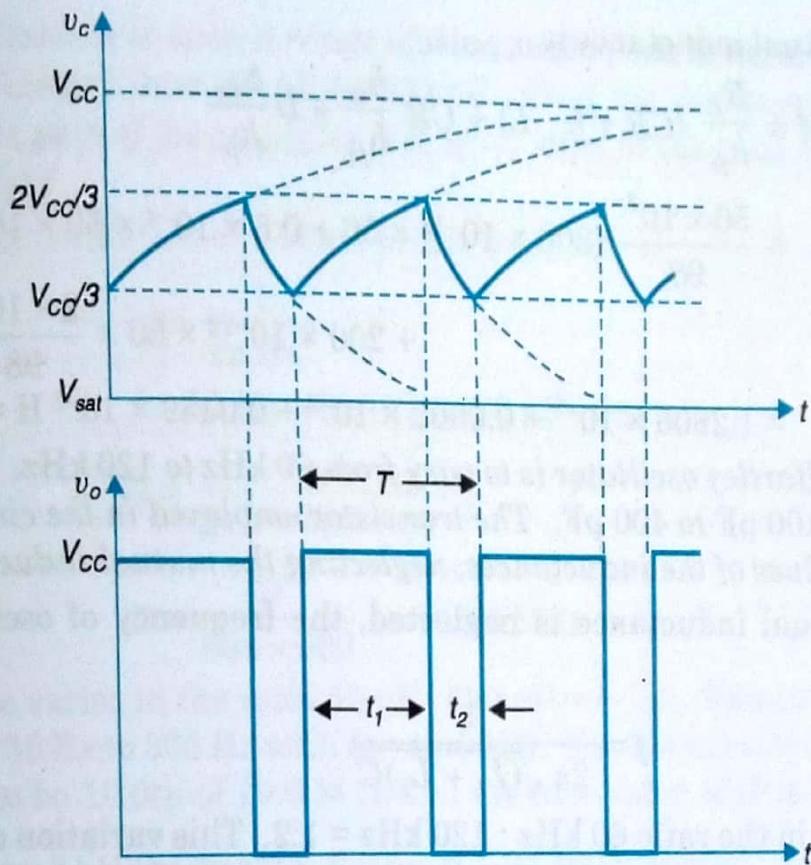Fig. 11.20 Variations of v_o and v_c with time, t .

At $t = t_1$, the flop-flop is reset, and C discharges through R_B and conducting Q_1 towards V_{sat} , obeying the following equation approximately :

$$v_C = \frac{2V_{CC}}{3} \exp\left(-\frac{t}{CR_B}\right) + V_{sat} \left[1 - \exp\left(-\frac{t}{CR_B}\right) \right]$$

In this equation, the former time t_1 is designated as $t = 0$. The equation is approximate since it is assumed that the transistor voltage stays at a constant value V_{sat} during the entire discharging interval. If $v_C = V_2 = V_{CC}/3$ at $t = t_2$ (with the instant t_1 taken as zero), we have

$$\frac{V_{CC}}{3} = \frac{2V_{CC}}{3} \exp\left(-\frac{t_2}{CR_B}\right) + V_{sat} \left[1 - \exp\left(-\frac{t_2}{CR_B}\right) \right]$$

or,

$$t_2 = CR_B \ln \frac{2V_{CC}/3 - V_{sat}}{V_{CC}/3 - V_{sat}}$$

If $V_{sat} \ll V_{CC}$, we obtain $t_2 \approx CR_B \ln 2 = 0.69 CR_B$.

The time period of the square waves for v_o is

$$T = t_1 + t_2 = 0.69 C (R_A + R_B) + 0.69 CR_B = 0.69 C (R_A + 2R_B)$$