

EXPERIMENT NUMBER - 36:-

TITLE:- Implement a 4-bit Asynchronous counter using 4013 IC.

OBJECTIVE:- Implement a 4-bit Asynchronous counter using D-Flip Flop IC (4013 IC).

APPARATUS REQUIRED:-

S. No.	Component's Name	Specification	QTY
1	D-Flip Flop IC	4013	2
2	Trainer Kit	-	1
3	Wires	-	1 bunch

THEORY:-



In a asynchronous counter, the flip-flop output transition serves as a source for triggering other flip flop. In other word, the count pulse inputs of all flip-flop (except first) are triggered not by the incoming pulses but rather by the transition that occurs in the other flip flop. It is also called ripple counter.

Name: Orunayan Bhattacharya Roll No.: 66

Section: CSB2C

Year: 2nd

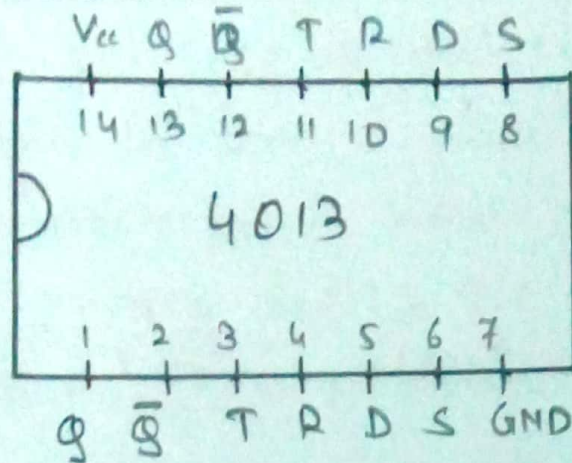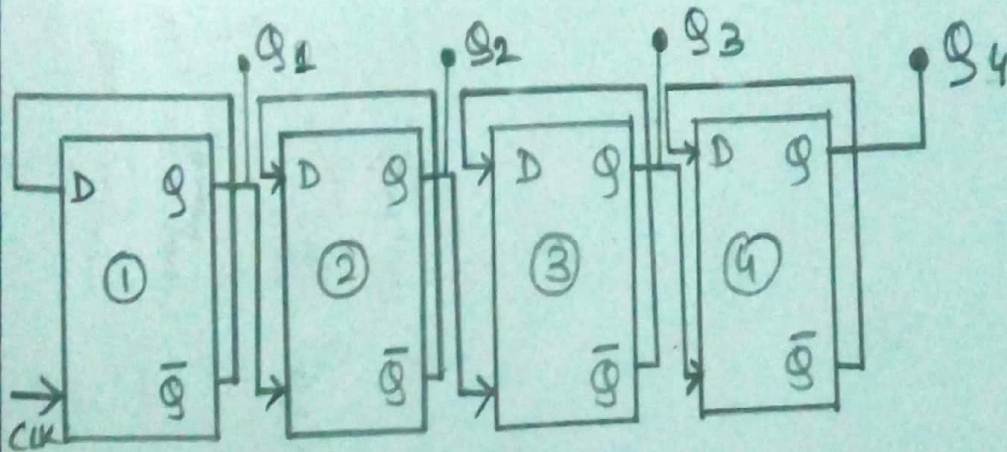

PIN CONFIGURATION :-CIRCUIT DIAGRAM :-OBSERVATION TABLE :-

Clock	Counter Output		State number	Decimal Counter output
	$Q_1$	$Q_2$		
Initially	0	0	—	0
1	0	1	1	1
2	1	0	2	2
3	1	1	3	3
4	0	0	4	0

Name : Drunayan  
Section : CSE2C

Roll No. : 66  
Year : 2<sup>nd</sup> (2017-18)



CONCLUSION:-

With the help of this experiment, we came to know about asynchronous counter and how we can construct it using 4013 IC or D-Flip Flop IC.

Name: Drunayan Bhattacharya Roll No.: 66  
Section: CSB2C Year: 2nd